



LAB 1 BOOLEAN ALGEBRA

CDA 3201C, Section 003



SEPTEMBER 24, 2019

PROFESSOR PETRIE
Summer Poissonnier
Z23492880

Name: Summer Poissonnier

Z#: 23492800 Grade: /100


1. [100] To get all your lab points you need to get your lab grader by the Teaching Assistant (TA) and submit under Canvas > Assignment > Lab 1 a **portfolio** consisting of one pdf file that includes:

- **Header:** Cover page or header with your name, my name, number, Logic Design class and class section
- **Handwork:** copy of planning work you did by hand (take picture of this worksheet or annotate this pdf with Edge)
- **Simulation:** a copy of the work you did in Altera Quartus
 - **Schematic** do all 3 circuits in one schematic window, must include comment with your name and Z#, the file name must include your name as part of the file name so it appears on the schematic screen window. You can take a picture of the screen or use Snipping Tool under Start menu to capture the pertinent part of the screen.
 - **Vector Waveform** simulation (simulated timing diagram) that include output for all 3 circuits in one screen
- **Wiring:** a picture of your breadboard with the wired circuit and your FAU OWL Card (if you got it graded in the lab also include with TA OWL card and the lab grade sheet in the background)

- 1.1 [10] Given the following Boolean Algebra Equation, complete the Truth Table at right

$$X = AB\bar{D} + ABD + C\bar{B}\bar{D} + \bar{A}BC\bar{D}$$

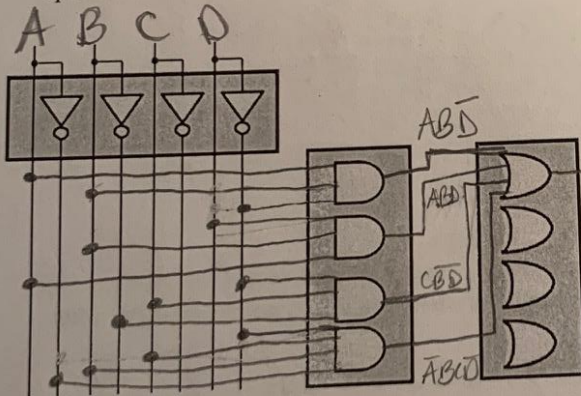- 1.2 [10] Utilizing the NOT AND OR gates provided below, label the input that you need to put through NOT, determine how many inputs are needed for each gate and use the number of gates you need (there may be extras). Draw the circuit connections to implement X exactly as specified.




ABCD	$AB\bar{D}$	ABD	$C\bar{B}\bar{D}$	$\bar{A}BC\bar{D}$	X
0000	001	000	011	1001	0
0001	000	001	010	1000	0
0010	001	000	111	1011	1
0011	000	001	110	1010	0
0100	011	010	001	1101	0
0101	010	011	000	1100	0
0110	011	010	101	1111	1
0111	010	011	100	1110	0
1000	101	100	011	0001	0
1001	100	101	010	0000	0
1010	101	100	111	0011	1
1011	100	101	110	0010	0
1100	111	110	001	0101	1
1101	110	111	000	0100	1
1110	111	110	101	0111	1
1111	110	111	100	0110	1

$$X = AB\bar{D} + ABD + C\bar{B}\bar{D} + \bar{A}BC\bar{D}$$

- 1.3 [10] Create a project in Altera Quartus called **lab1-PETRIE-yourlastname** following Dr. Petrie's step by step guide and verify the circuit you designed in 1.2 works according to 1.1 Truth Table. If it does not work as specified by the Truth Table, then determine if error is in the Truth Table or your design. Create with same name a Block Diagram/Schematics (.bdf) of your design in 1.3. Is there a 4-input OR gate available? If there is not then figure out how you will change the design using 2 input OR gates. Generate with same name a Waveform file (.vwf), group the inputs and set the counter to step through all the values, Compile, and Simulate. Make sure to save the project, the .bdf and .vwf files often. Check the .vwf to verify it produces same results as the Truth Table 1.1. Keep the project and files to expand the Block Diagram to include the other 2 circuits in the rest of lab 1.

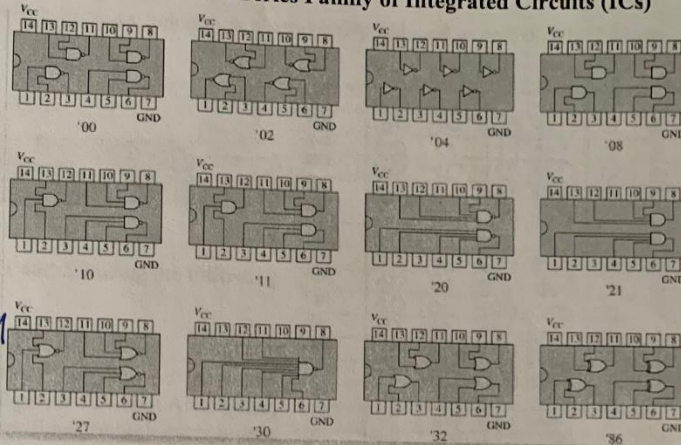
1.4 [5] Gates are packaged in ICs. Determine which and how many ICs from the 7400 Series family at right you will need to implement the circuit as you specified in 1.3 (Note there are no 4 input ORs in your kit so use 2 input OR ICs instead:

The 7400 Series Family of Integrated Circuits (ICs)



Quantity needed?	7400 Series IC #
1	7410 → 7411
1	7432
1	7404
1	7421

 1.5 [10] Plan out the layout by labeling inputs and outputs of the gates or drawing the wiring use blue-A, Green-B, Brown-C, Orange-D, use the same color dashed wire for NOT. Note we don't have 4 input ORs in the kit, so we need to make due with using 2 input ORs:



1.6 [8] Look at the handout on Boolean Algebra Postulates and Theorems. Identify by either by writing the name or the equation of the postulate(s) or theorem(s) used to simplify.

$$\begin{aligned}
 X &= AB\bar{D} + ABD + C\bar{B}\bar{D} + \bar{A}BC\bar{D} \\
 &\stackrel{\text{Factoring}}{=} AB(\bar{D} + D) + (\bar{B} + \bar{A}B)C\bar{D} \\
 &\stackrel{\text{Additive Complement}}{=} AB(1) + (\bar{B} + \bar{A}B)C\bar{D} \\
 &\stackrel{\text{Multiplicative Identity}}{=} AB + (\bar{B} + \bar{A}B)C\bar{D} \\
 &\stackrel{\text{DeMorgan's Law}}{=} AB + (\bar{B} + \bar{A}B)C\bar{D} \\
 &\stackrel{\text{Distribution}}{=} AB + \bar{B}C\bar{D} + \bar{A}BC\bar{D} \\
 &\stackrel{\text{Absorption}}{=} AB + \bar{B}C\bar{D} + \bar{A}BC\bar{D} \\
 &\stackrel{\text{Absorption}}{=} AB + \bar{B}C\bar{D} + \bar{A}BC\bar{D}
 \end{aligned}$$

Name:

Z#:

Grade: /100


As you verified in 1.a.6, the following Boolean function is algebraically reduced to two different forms denoted as X1 and X2 as follows.

$$\begin{aligned} X &= AB\bar{D} + AB\bar{D} + C\bar{B}\bar{D} + \bar{A}BC\bar{D} \\ &= AB(\bar{D} + D) + (\bar{B} + \bar{A})C\bar{D} \\ &= AB + (\bar{B} + \bar{A})C\bar{D} = \underline{AB + \bar{B}C\bar{D} + \bar{A}C\bar{D}} = X1 \\ \text{or } &= AB + (\bar{A}\bar{B})C\bar{D} = \underline{AB + C\bar{D}} = X2 \end{aligned}$$

ABCD	AB	C \bar{D}	$\bar{B}C\bar{D}$	$\bar{A}C\bar{D}$	X1	X2
0000	00	01	101	101	0	0
0001	00	00	100	100	0	0
0010	00	11	111	111	1	1
0011	00	10	110	110	0	0
0100	01	01	001	101	0	0
0101	01	00	000	100	0	0
0110	01	11	011	111	1	1
0111	01	10	010	110	0	0
1000	10	01	101	001	0	0
1001	10	00	100	000	0	0
1010	10	11	111	011	1	1
1011	10	10	110	010	0	0
1100	11	01	001	001	1	1
1101	11	00	000	000	1	1
1110	11	11	011	011	1	1
1111	11	10	010	010	1	1

1.7) [5] Verify the equivalence of X1 and X2 using the following truth table:

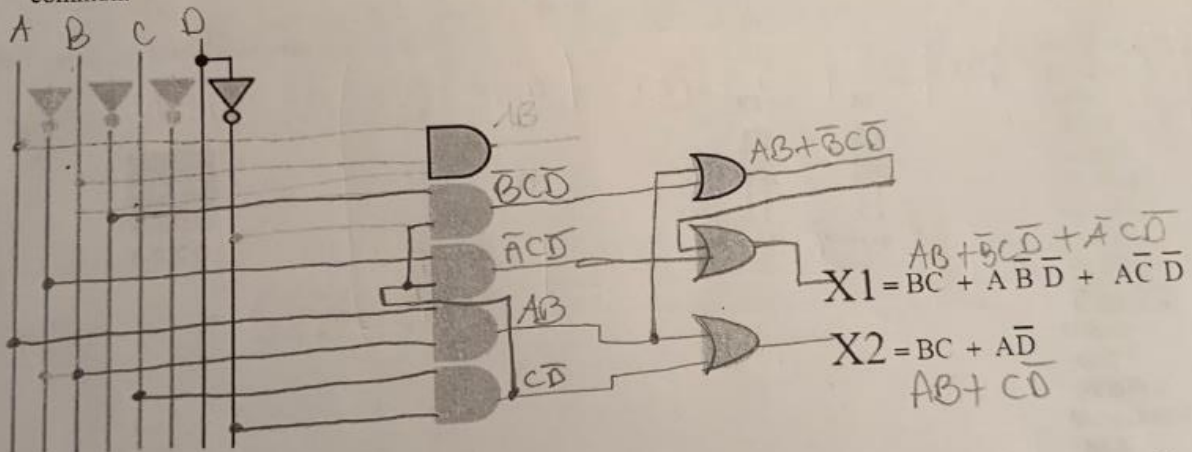1.8) [7] Design the circuit for the above two reduced functions, X1 and X2, using exactly 3 NOT gates, 4 2-input AND gates, 3 2-input OR gates. Note, there will not enough gates unless you are able to reuse by finding things both equations have in common.



1.9) [10] Verify the circuit design/behavior by implementing the circuit using Quartus before you actually build the circuit on the breadboard. Open the Quartus project you build in 1.a.3 and add the X1 and X2 circuits to the X circuit Block Diagram / Schematics. Add the X1 and X2 inputs to the Waveform File and Compile and Simulate, check if all $X = X1 = X2$. You will show the TA you have these files and submit the .bdf and .vwf to the Lab 1 together with the scan of this completed Lab with all your work. Dr. Petrie will adjust your grade – these 2 points will be converted to 20 points total for this section and 1.a.3.

Name: _____

Lab Assignment


1

Z#: _____

Grade: _____

/100

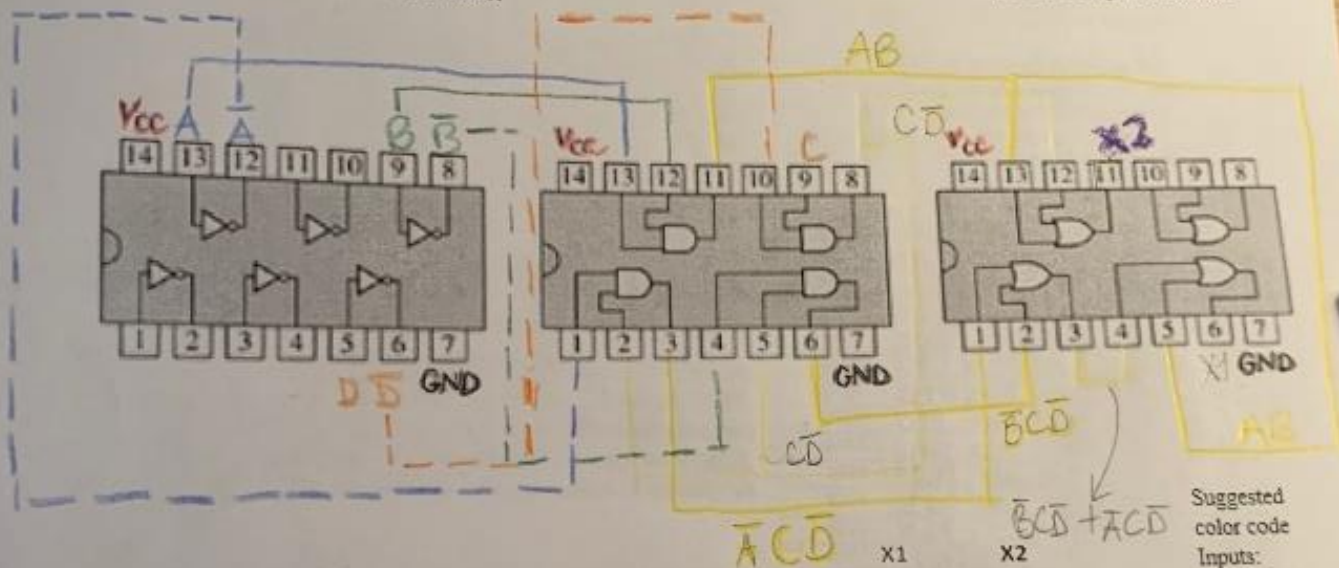- 1.10) [20] Use the following chip pin-out to conveniently plan your wiring to build the above 2-output circuit for X1 and X2 on your breadboard using exactly 1/2 7404, 1 7408 and 3/4 7432 chips on your breadboard and then connect inputs ABCD to 4 DIP switched and the outputs X1 X2 to two LED indicators. Test all the 16 different input combinations and observe the two outputs to be equivalent and matching the 1.7 Truth Table.




ABCD



Suggested color code
Inputs:
BLUE
GREEN
BROWN
ORANGE
In-Between:

WHITE
YELLOW

Outputs:
GREY
PURPLE
Vcc and GND:
RED
BLACK

Note that  = white!!

After you get it to work but before the TA grades it, take a picture of your breadboard to submit as part of Lab 1 documentation. After it is graded take a picture of the gradesheet, then, except for the ground and power wires, pull the wires attached to the three the three ICs on the upper breadboard you used for this experiment (Do NOT pull the lab platform wires just the ones in the upper breadboard), leaving the three ICs plugged into your board with power and ground connected. **KEEP THE WIRE TO REUSE FOR NEXT LAB.** Upload the portfolio of your labwork to Canvas to validate your lab grade.

Summer Poissonnier

Lab 1



Petrie Section 003

$X = ABD' + ABD + CB'D' + A'BCD'$

$X1 = AB + B'CD' + A'CD'$

$X2 = AB + CD'$


September 25, 2019

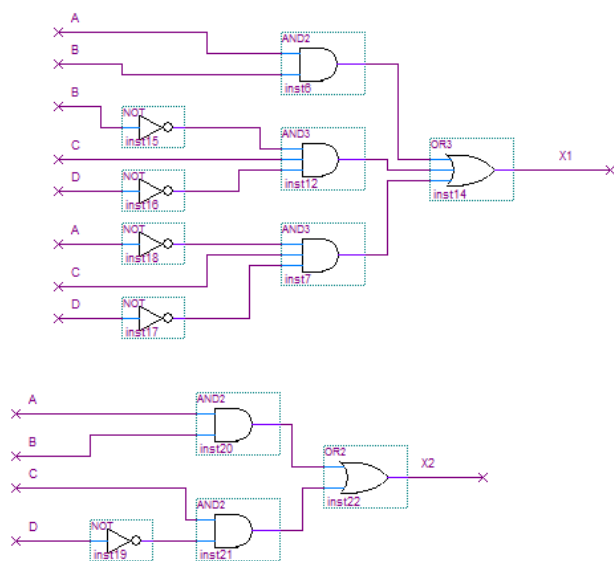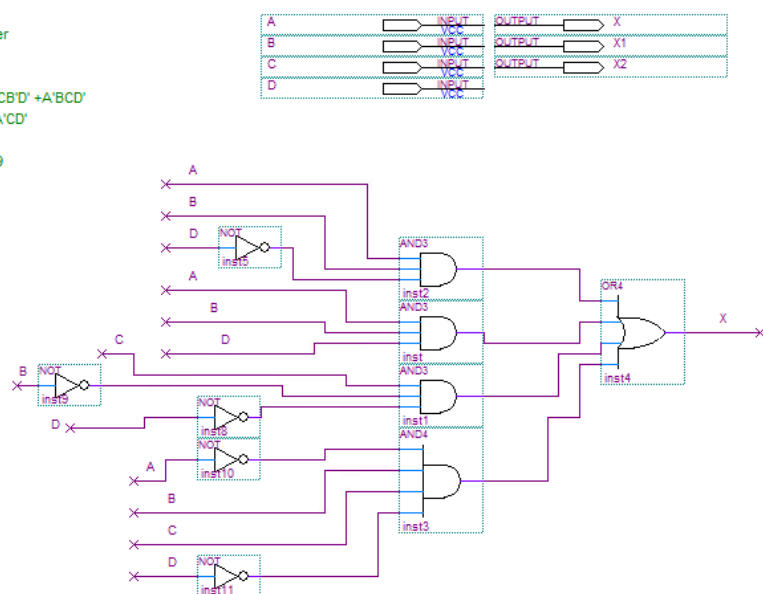


Master Time Bar: 15.6 ns

Pointer: 236.8 ns

Interval: 22

 

 


Name: Summer Poissonnier Z#23492880 x Summer Poissonnier

CERTIFICATE OF AUTHENTICITY
000-71872
GUARANTEED 100% ORIGINAL DESIGN
DO NOT REMOVE OR TAMPER WITH SEAL

Logic Lab Grading Rubric

Lab#	Title	Time (wks)	Bench	Pre-Work	Quartus	Schematic	Wiring Diagram	Used Many Colored Wires	Working	Bonus	Cleaned up	SCORE (100%)	Date & Time	TA Name & Initials
Lab 6 Only														
0	Infrastructure & Demo: Hexadecimal 7Segment Display & New And Or NAND Gates	1						✓	✓	✓	✓	100%	8/15 5:14	David Wilson MW
1	Boolean Simplification & Quartus	1			50%	25% for Logic Gates only	10%	5%	10%	10%	Non (1-20%)			
2	2 Digit Counter			✓	✓	✓	✓	✓	✓	✓	✓	100%	09/27/19 10:56 am	Eric Oster
Lab 2+			10%	10%	25%	10%	10%	5%	40%	10%	Non (1-20%)			
2	Adder - NAND	2												
3	Decoder: 1 Segment of 7Seg. Display	2												
4	Flip-Flop #1	2												
5	Flip-Flop #2	2												
6	2 Digit Counter: 2 Decade Counters & Mux	2												



 

Name: Summer Poissonnier Z#2349 2880 X Summer Poissonnier

CERTIFICATE OF AUTHENTICITY
000-71872

Logic Lab Grading Rubric

Lab#	Title	Time (wks)	Bench	Pre-Work	Quartus	Schematic	Wiring Diagram	Used Many Colored Wires	Working	Bonus	Cleaned up	SCORE (100%)	Date & Time	TA Name & Initials
Lab 0 Only														
1	Infrastructure & Demo: Hexadecimal Input/Output Display & Not And Or NAND Gates	1						10% for Logic Gates only	✓	✓	✓	100%	9/15 5:14	David Wilton
2	Boolean Simplification & Quartus	1			60%	25% for Logic Gates only	10%	5%	10%	10%	Non (-20%)	100%	09/27/19 10:56am	Eric Oster
Lab 2+			10%	10%	25%	10%	10%	5%	40%	10%	Non (-20%)			
3	Adder - NAND	2												
4	Decoder: 1 Segment of 7Seg Display	2												
5	Flip-Flop #1	2												
6	Flip-Flop #2	2												
7	2 Digit Counter: 2 Decade Counters & Mux	2												



Summer Poissonier

Z#23492880

X

James Patterson

I affirm that I have performed the following work:

**CERTIFICATE
OF AUTHENTICITY**

000-71872

GUARANTEED ORIGINAL AND GENUINE
DO NOT REMOVE OR TAMPER SEAL

000-71872

Logic Lab Grading Rubric

[illegible]